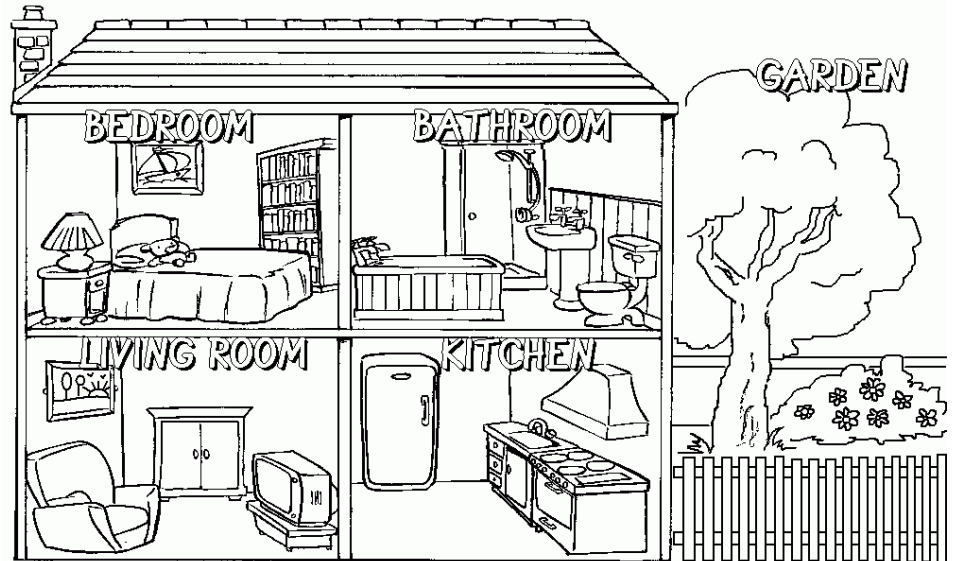


# Electric House Project

Due date 04/07/2016

**Objectives:** Design and construct both series and parallel circuits as used in electrical circuits in homes by creating a model house with circuit diagram and working circuits.

You may work with a partner to make a shoebox-sized house wired with the required circuits. Adding décor and furnishings will show your awareness of the appropriate uses of each type of circuit.



## Requirements:

Design and construct your electric house project with any school appropriate theme and in any way you like, within these guidelines:

Your project house must have at least two rooms (or definitive spaces) connected by a doorway or passage

Your project house must be at least 4" x 6" x 1" (close to the size of a shoebox)

Your project house must have the following circuits in these separate spaces:


1. **A series circuit room:** two lights in series with a switch in one room
2. **A parallel circuit room:** three lights in parallel with a switch in one room

Your building must display a circuit diagram.

3D objects should be included appropriate for the type of room; wall coverings should be used to add interest.
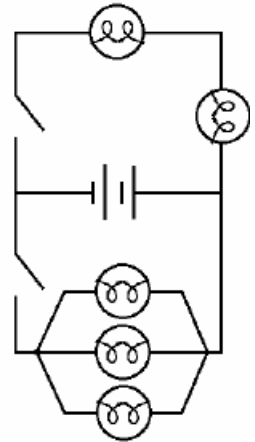
## Construction

- Recommended materials may include cardboard, foamboard, shoeboxes, etc.
- Some materials such as insulated wire, holiday lights, brads, and paperclips will be available during building sessions before or after school.
- Switches can be made from brads and paper clips.
- Your project house will be powered by a 9V battery. You will need two leads to attach the battery.
- Each circuit must be able to work independently from the other as well as both circuits on at the same time without moving the battery
- You will need access to scissors, wire cutters and wire strippers.
- Furnishings may **not** be premade toys such as legos: everything must be made for this project. Suitable materials for furniture include but are not limited to origami, wood, modeling clay, plastic, etc.



## Grading Rubric

Category	Points available	Points scored
Project submitted on time	0-10 pts	
Followed instructions for size and materials	0-20 pts	
Switch operates in each room	0-10 pts	
Series circuits with 2 lights wired correctly	0-15 pts	
Parallel circuit with 3 lights wired correctly	0-15 pts	
Series and parallel circuits work independently without moving battery	0-15 pts	
Effort, creativity, neatness	0-15 pts	

**Your project is due by the time your class begins on the due date whether or not you are present at school.**

**Your grade will be reduced by 25 points for each day the project is late.**

Here is a link to another teacher's past projects so you can see what earns an "A". You tube link on how to make a switch.

<http://pleasanton.k12.ca.us/avhsweb/barnettredyfass/Physics/ProjectExamples/ExElectricHouse.htm>